

Verification of Digital Systems, Spring 2018

J. A. Abraham

Homework No. 4

Assigned: 03/09/19 Due: 03/25/19

Total Points: 200

1. **[Symbolic Model Checking]** Answer the following questions based on this module definition:

```
module fair_arbiter(  
  
    input clk,  
    input rst_n,  
    input req0,  
    input req1,  
    output reg grant0,  
    output reg grant1  
);  
always @(posedge clk or negedge rst_n)  
    if (!rst_n)  
        begin  
            grant0 <= 0;  
            grant1 <= 1;  
        end  
    else  
        begin  
            grant0 <= req0 && ((!req1) || ((!grant0) && grant1));  
            grant1 <= req1 && ((!req0) || ((!grant1) && grant0));  
        end  
    assert property(!(grant0 && grant1));  
endmodule
```


- (a) (15 Points) Describe some safety properties of this arbiter?
- (b) (15 Points) Describe some liveness properties of this arbiter?
- (c) (40 Points) Will the assert property mentioned in the code be satisfied? Use symbolic model checking to formally prove your answer.
2. **[Term Rewriting]** Consider the set of terms as (2NOR(), A, B, C, a, b, \neg , \vee , \wedge)
- (a) (10 Points) Write a set of rules for a 2-input NOR.
- (b) (20 Points) Apply the above rules to rewrite a 3-input NAND: $(\neg(A \wedge B \wedge C))$ using only 2NOR().
3. **[Data Representation]** (10 Points) We have n pigeons and m holes where (m=n-1). Each pigeon must be placed in a hole and no two pigeons must be placed in the same hole. Write the safety and liveness property of this trivial problem and represent both of them as a CNF (no other formats will be accepted.). Also state why SAT solvers would find it difficult to find a satisfying interpretation for this problem.
(Use $P_{a,b}$ to represent putting pigeon a in hole b.)

4. **[Data Representation] (15 Points)** Write the CNF formulating representing the *one-hot* condition on the bits of the vector

$$X_1, X_2, X_3, X_4, X_5$$

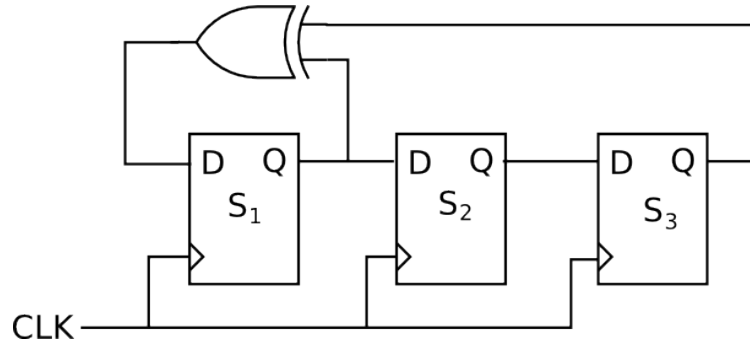5. **[Representing State Machines]** Consider the Pseudo-Random Sequence generator circuit below with current state $V = \langle S_1, S_2, S_3 \rangle$ and next state $V' = \langle S'_1, S'_2, S'_3 \rangle$. Assume that the initial state of PN sequence generator is

$$I(V) = \langle S_1 = 1, S_2 = 0, S_3 = 0 \rangle$$



- (a) **(15 Points)** Write the equations for the transition function for S'_1, S'_2 and S'_3
- (b) **(10 Points)** Write the equation for the Transition Relation, $\tilde{T}(V, V')$ (you may use the \iff function).
- (c) **(40 Points)** Which state of the Pseudo-Random Sequence Generator is not reachable. Prove your answer using symbolic model checking.
- (d) **(10 Points)** What happens if the circuit is in the unreachable state? Write a SystemVerilog Assertion for checking this condition.